
Problems and Solutions

in Mathematics, Physics and Applied Sciences

compiled by C. Bond

Vol.1 no.23

Design Notes: RC Phase Shift Oscillator

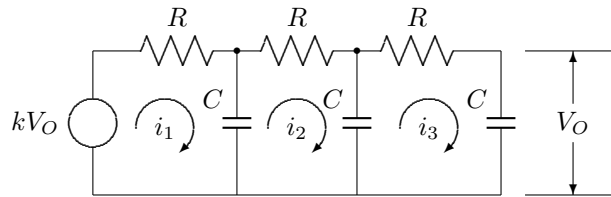


Figure 1: RC Phase Shift Network

The RC network above, when configured as shown, will oscillate at a characteristic frequency if the amplifier gain is sufficient. The amplifier, indicated as a generator on the left of the diagram, is a voltage controlled voltage source (VCVS) driven by the output voltage V_O .

This note suggests a simple method for determining the oscillating frequency, f , and required gain, k , in terms of the circuit elements.

The first step is to write out the network equations in matrix form. This gives:

$$\begin{vmatrix} R + 1/sC & -1/sC & 0 \\ -1/sC & R + 2/sC & -1/sC \\ 0 & -1/sC & R + 2/sC \end{vmatrix} \begin{vmatrix} i_1 \\ i_2 \\ i_3 \end{vmatrix} = \begin{vmatrix} kV_O \\ 0 \\ 0 \end{vmatrix}$$

Symbolically, this is equivalent to

$$\mathbf{Z} \cdot \mathbf{I} = \mathbf{V}$$

The RC network produces a phase lag and, to get the positive feedback required for oscillations, we will use an inverting amplifier and find the frequency corresponding to a 180 degree lag. The attenuation at this frequency sets a lower bound on the gain needed to sustain the oscillations.

Solving for current i_3 ,

$$i_3 = \frac{\begin{vmatrix} R + 1/sC & -1/sC & kV_O \\ -1/sC & R + 2/sC & 0 \\ 0 & -1/sC & 0 \end{vmatrix}}{\Delta} \quad (1)$$

$$= \frac{kV_O}{s^2C^2\Delta} \quad (2)$$

where Δ is the determinant of the impedance matrix, \mathbf{Z} . But $i_3 = V_O \cdot sC$ so,

$$s^3C^3\Delta = k \quad (3)$$

$$s^3R^3C^3 + 5s^2R^2C^2 + 6sRC + 1 = k \quad (4)$$

Substituting $j\omega$ for s and collecting real and imaginary parts,

$$(1 - 5\omega^2R^2C^2) + j\omega RC(6 - \omega^2R^2C^2) = k. \quad (5)$$

Setting the imaginary part to 0 and solving for ω

$$\omega = \frac{\sqrt{6}}{RC}.$$

Substituting this value in the real part of (5),

$$k = -29. \quad (6)$$

Hence, the circuit will oscillate at frequency $f = \omega/2\pi$. The amplifier must be in an inverting configuration (negative sign) and have a gain of (at least) 29, in order to support oscillations.